# **The Fulltone Fulldrive2**

This was drawn to figure out how to convert a Fulldrive2 into a Bassdrive. Grunt work by BP, hard stuff and mod suggestions by cd.

## The story.

I got a FD2 in trade and used it with my bass, it sounded great, smooth creamy tone, from lightly warmed to pretty gosh darn fuzzy and enough knobs to dial in your own picky tastes. Then I read on the website that there is a version with an extra octave of low end, I had to have it. Off to the internet where I found someone who could tell me how to mod for the extra octave if they could see the schematic, so I learned to draw and we all lived happily ever after.

### The Mods

If you want the equivalent of a Bass-Drive, change C6 to .22uf or .33uf and C8 to .8uf. C1 is only for pop-prevention when the Boost switch is engaged.

Besides that, no other mods should be necessary to let in all the low frequencies. The input cap (.02u) is large enough to let all frequencies through. Same with the output caps. Increasing C8 may not be necessary actually, increasing it will increase the low end which will sound like a high end cut (slight difference).





#### Parts list

What we have here are the actual DMM readings and what I could read on the parts. The schematic has standard values substituted for these resistors.

- R1 21.8k red red orange gold R2 - 21.6k red red orange gold R3 - 17.6k purple grey orange gold R4 - 46.4k yellow purple orange gold R5 - .98k brown black red gold R6 - .98k brown black red gold R7 - .22k red red purple gold R8 - 9.8k brown black orange gold R9 - 9.8k brown black orange gold R10 - 9.8k brown black orange gold R11 - 4.6k purple red gold R12 - Jumper R13 - 1.01meg brown black blue gold R14 - 1k brown black red gold R15 - 9.7k brown black orange gold R16 - 9.8k brown black orange gold R17 - 81.4k grey red orange gold R18 - .987 meg brown black blue gold R19 - 99.1 ohm brown black brown gold R20 - 9.8k brown black orange gold R21 - 4.6k purple red gold R22 - 146.5k purple blue gold
- C1 2a103kt
- C2 10uf
- C3 100uf
- C4 1uf
- C5 2a224k tracon
- C6 1h104k tracon
- C7 1uf
- C8 2a224k tracon
- C9 1h203kt
- C10 ceramic, says simply 10
- C11 100uf
- C12 10uf
- C13 1h104 tracon
- C14 unknown, under epoxy, a 1996 schematic says 51pf
- IC JRC 4558D
- Q1, Q2 C828 R25
- VR1 936k DI YA 0333
- VR2 -503k DI YA 0331 VR3 - 25k - DI YA 0329
- VR4 88k DI YA 0342
- D1 1N\*\*\*5 (all I could read) D2, D3 - These are under epoxy and are asymetric with voltage drops of .584 & .607v

Switch 1 - DPDT on on on



Blue lines are insulated and only connect where you see a •



#### Notes:

 all resistor values confirmed via multimeter. Cap values taken from cap markings (unmeasured)
cap in feedback loop and clipping diodes are under epoxy, these values are probable guesses (voltage drop of diodes is .584∨ and .607∨)

 S1 is the Vintage/FM/Comp-Cut switch (ON-ON-ON). The Vintage and Comp-Cut modes are shown, however in the FM mode BOTH sides of the DPDT are shorted (not shown). If you ignore the comp-cut feature, in Vintage mode the 47k/.01u combination is NOT connected to pin 7; in FM mode the combination is connected to pin 7 (see frequency response graph above).